
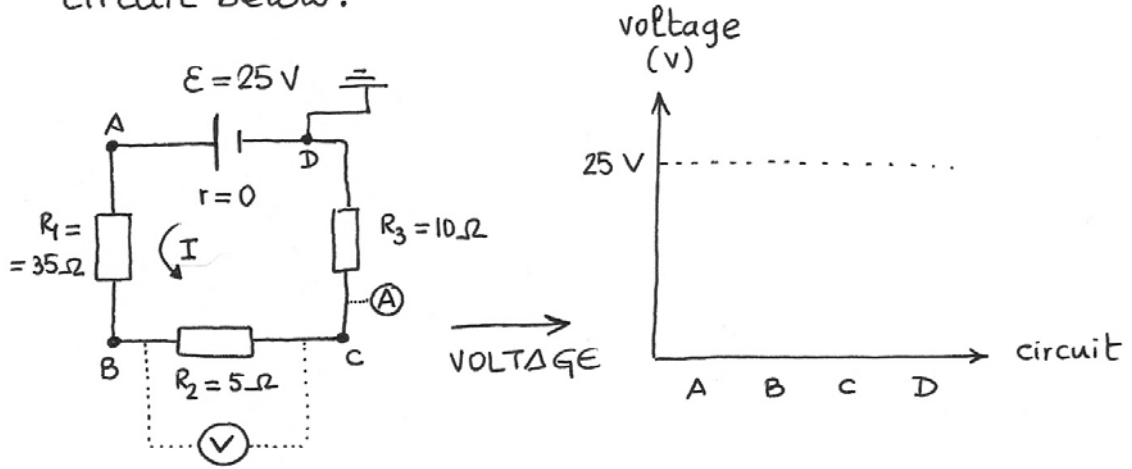


Conceptual Exercise

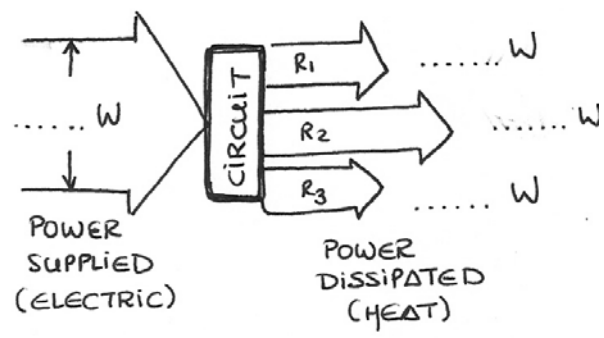Complete the graphics related to the electric circuit below:



POWER



READINGS

