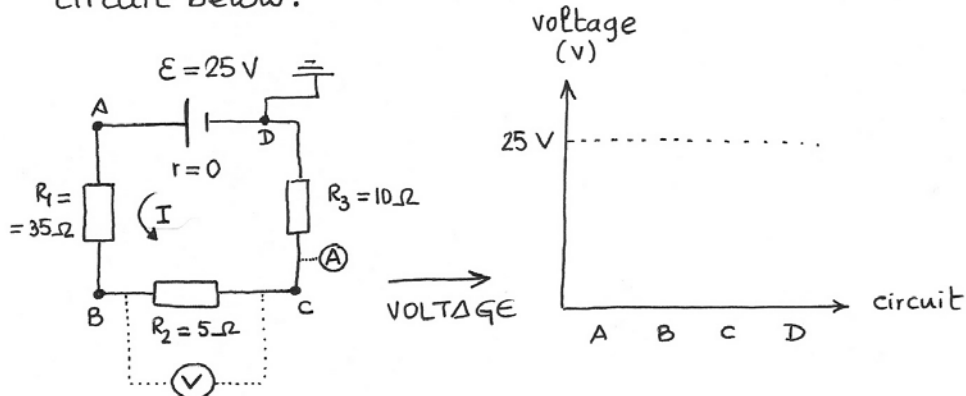


Conceptual Exercise

Complete the graphics related to the electric circuit below:



Determination of potentials (voltages)

"D" point is connected to the ground. Therefore, $V_D = 0\text{ V}$

"A" point is next to the positive electrode of the battery. It means that $V_A = 25\text{ V}$

The potential difference between "A" and "B" (the voltage "lost") is:

$$V_A - V_B = I * R = I * 35\ \Omega$$

To get the value, we need the value of the current. That can be found applying Ohm's law:

$$I = \frac{\mathcal{E}}{R_{\text{equiv}}} = \frac{25\text{ V}}{35\ \Omega + 5\ \Omega + 10\ \Omega} = 0.5\text{ A}$$

The potential (voltage) difference between "A" and "B" is:

$$V_A - V_B = I * R = 0.5\text{ A} * 35\ \Omega = 17.5\text{ V}$$

The potential (voltage) at "B" is:


$$V_A - V_B = 17.5\text{ V} \xrightarrow{V_A = 25\text{ V}} 25\text{ V} - V_B = 17.5\text{ V} \rightarrow V_B = 7.5\text{ V}$$

The potential difference between "B" and "C" is:

$$V_B - V_C = I * R = 0.5\text{ A} * 5\ \Omega = 2.5\text{ V}$$

The potential (voltage) at "C" is:
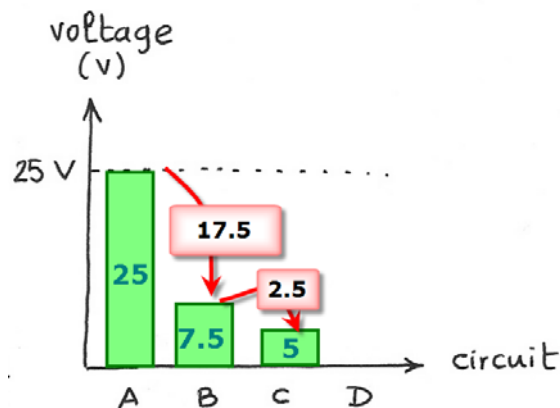
$$V_B - V_C = 2.5\text{ V} \xrightarrow{V_B = 7.5\text{ V}} 7.5\text{ V} - V_C = 2.5\text{ V} \rightarrow V_C = 5\text{ V}$$



Determination of powers

The electric power (energy per second) supplied by the battery is:


$$P_{\text{supplied}} = \varepsilon * I = 25 \text{ V} * 0.5 \text{ A} = 12.5 \text{ W}$$

The power dissipated (as heat) by each resistor is:

$$P_{R1} = I^2 * R = (0.5 \text{ A})^2 * 35 \Omega = 8.75 \text{ W}$$

$$P_{R2} = I^2 * R = (0.5 \text{ A})^2 * 5 \Omega = 1.25 \text{ W}$$
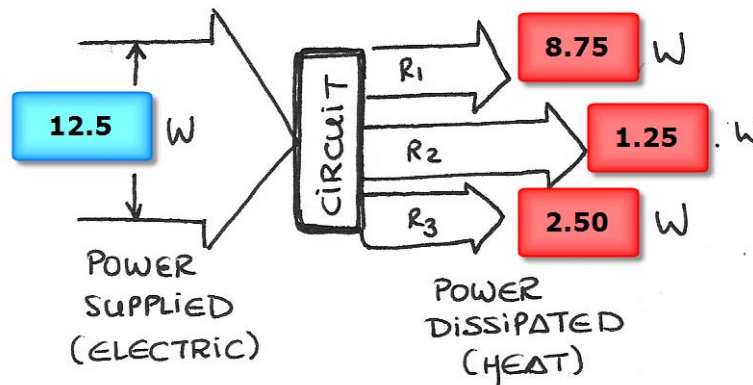
$$P_{R3} = I^2 * R = (0.5 \text{ A})^2 * 10 \Omega = 2.50 \text{ W}$$



Determination of the readings

The reading of the ammeter gives the value of the current. The reading of the voltmeter gives the value of the potential difference between two points:

