

Conceptual Exercise

Complete the graphics related to the electric circuit below:

