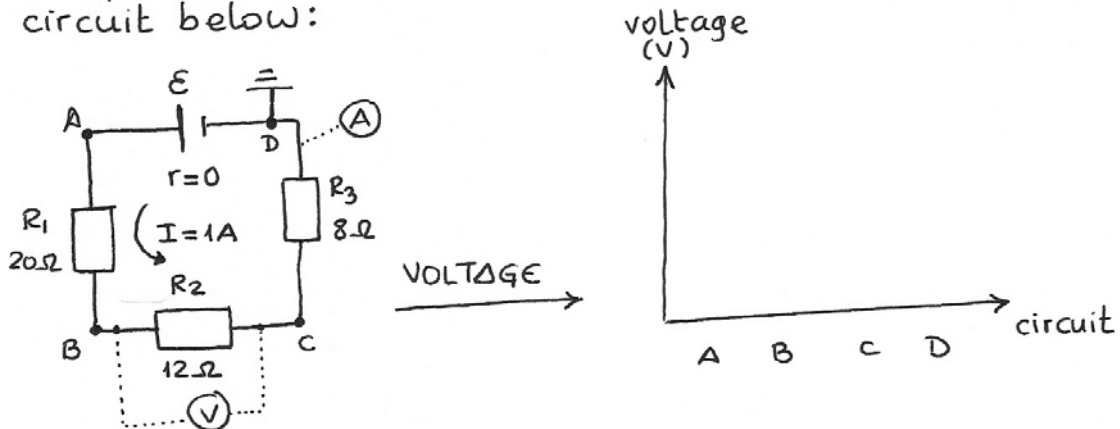


Conceptual Exercise

Complete the graphics related to the electric circuit below:



Determination of potentials (voltages)

"D" point is connected to the ground. Therefore, $V_D = 0 \text{ V}$

From Ohm's Law, we can get the electromotive force of the battery:

$$I = \frac{\varepsilon}{R_{\text{equiv}}} = \frac{\varepsilon}{20 \Omega + 12 \Omega + 8 \Omega} = 1 \text{ A} \rightarrow \varepsilon = 40 \text{ V}$$

"A" point is next to the positive electrode of the battery. It means that $V_A = 40 \text{ V}$

The potential difference between "A" and "B" (the voltage "lost") is:

$$V_A - V_B = I * R = 1 \text{ A} * 20 \Omega = 20 \text{ V}$$

The potential (voltage) at "B" is:


$$V_A - V_B = 20 \text{ V} \xrightarrow{V_A = 40 \text{ V}} 40 \text{ V} - V_B = 20 \text{ V} \rightarrow V_B = 20 \text{ V}$$

The potential difference between "B" and "C" is:

$$V_B - V_C = I * R = 1 \text{ A} * 12 \Omega = 12 \text{ V}$$

The potential (voltage) at "C" is:
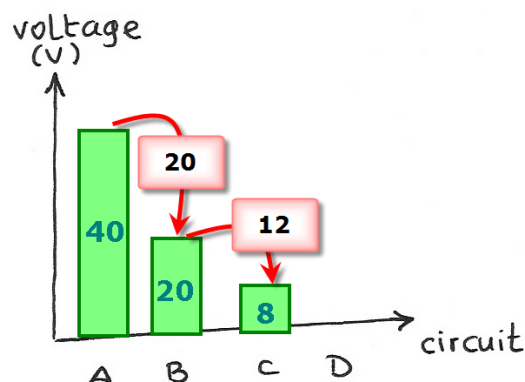
$$V_B - V_C = 12 \text{ V} \xrightarrow{V_B = 20 \text{ V}} 20 \text{ V} - V_C = 12 \text{ V} \rightarrow V_C = 8 \text{ V}$$



Determination of powers

The electric power (energy per second) supplied by the battery is:


$$P_{\text{supplied}} = \varepsilon * I = 40 \text{ V} * 1 \text{ A} = 40 \text{ W}$$

The power dissipated (as heat) by each resistor is:

$$P_{R1} = I^2 * R = (1 \text{ A})^2 * 20 \Omega = 20 \text{ W}$$

$$P_{R2} = I^2 * R = (1 \text{ A})^2 * 12 \Omega = 12 \text{ W}$$
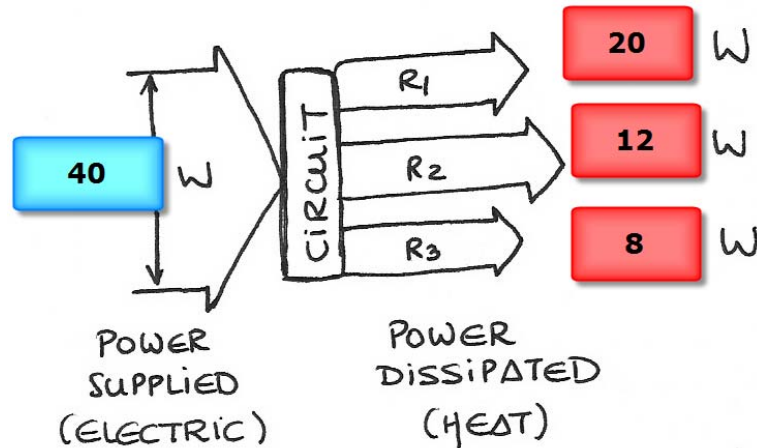
$$P_{R3} = I^2 * R = (1 \text{ A})^2 * 8 \Omega = 8 \text{ W}$$



Determination of the readings

The reading of the ammeter gives the value of the current. The reading of the voltmeter gives the value of the potential difference between two points:

