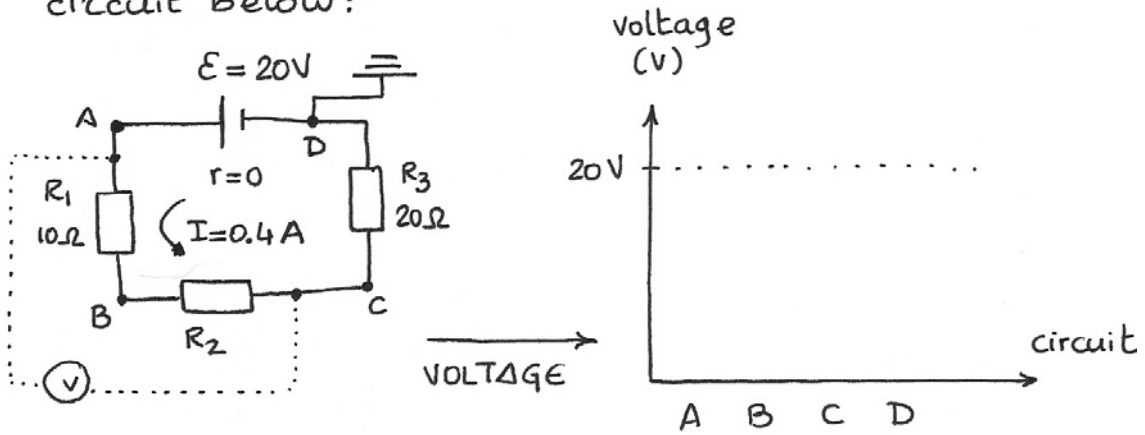


## Conceptual Exercise

Complete the graphics related to the electric circuit below:



### Determination of potentials (voltages)

"D" point is connected to the ground. Therefore,  $V_D = 0\text{V}$

"A" point is next to the positive electrode of the battery. It means that  $V_A = 20\text{V}$

From Ohm's Law, we can get the value of  $R_2$ :

$$I = \frac{\mathcal{E}}{R_{\text{equiv}}} = \frac{20\text{V}}{10\Omega + R_2 + 20\Omega} = 0.4\text{A} \rightarrow R_2 = 20\Omega$$

The potential difference between "A" and "B" (the voltage "lost") is:

$$V_A - V_B = I * R = 0.4\text{A} * 10\Omega = 4\text{V}$$

The potential (voltage) at "B" is:


$$V_A - V_B = 4\text{V} \xrightarrow{V_A = 20\text{V}} 20\text{V} - V_B = 4\text{V} \rightarrow V_B = 16\text{V}$$

The potential difference between "B" and "C" is:

$$V_B - V_C = I * R = 0.4\text{A} * 20\Omega = 8\text{V}$$

The potential (voltage) at "C" is:
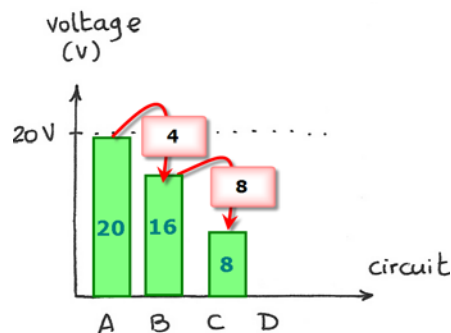
$$V_B - V_C = 8\text{V} \xrightarrow{V_B = 16\text{V}} 16\text{V} - V_C = 8\text{V} \rightarrow V_C = 8\text{V}$$



### Determination of powers

The electric power (energy per second) supplied by the battery is:


$$P_{\text{supplied}} = \varepsilon * I = 20 \text{ V} * 0.4 \text{ A} = 8 \text{ W}$$

The power dissipated (as heat) by each resistor is:

$$P_{R_1} = I^2 * R = (0.4 \text{ A})^2 * 10 \Omega = 1.6 \text{ W}$$

$$P_{R_2} = I^2 * R = (0.4 \text{ A})^2 * 20 \Omega = 3.2 \text{ W}$$
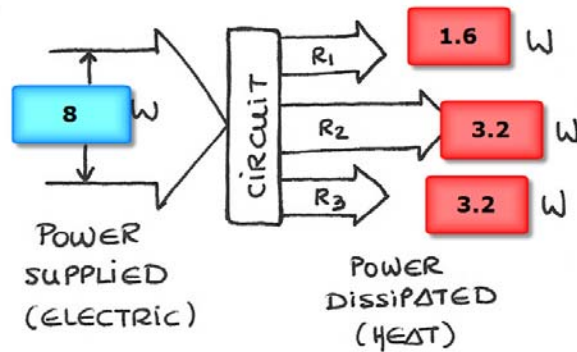
$$P_{R_3} = I^2 * R = (0.4 \text{ A})^2 * 20 \Omega = 3.2 \text{ W}$$



### Determination of the readings

The reading of the ammeter gives the value of the current. The reading of the voltmeter gives the value of the potential difference between two points:

