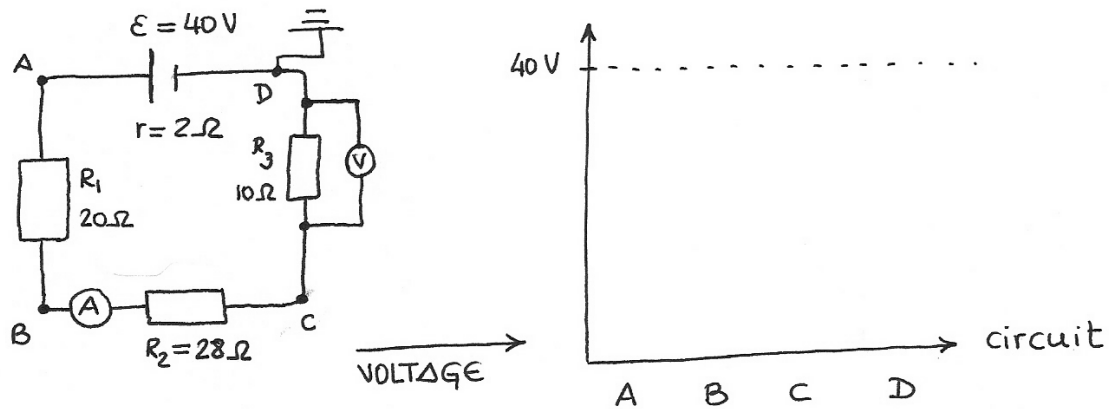


## Conceptual Exercise

Complete the graphics related to the electric circuit below:



### Determination of potentials (voltages)

"D" point is connected to the ground. Therefore,  $V_D = 0\text{ V}$

"A" point is next to the positive electrode of the battery, but the charges need to overcome the internal resistance.

From Ohm's Law, we can get the value of I:

$$I = \frac{\mathcal{E}}{R_{\text{equiv}}} = \frac{40\text{ V}}{2\ \Omega + 20\ \Omega + 28\ \Omega + 10\ \Omega} = 0.67\text{ A}$$

It means that  $V_A = 40\text{ V} - 2\ \Omega * 0.67\text{ A} = 38.66\text{ V}$

The potential difference between "A" and "B" (the voltage "lost") is:

$$V_A - V_B = I * R = 0.67\text{ A} * 20\ \Omega = 13.4\text{ V}$$

The potential (voltage) at "B" is:


$$V_A - V_B = 13.4\text{ V} \xrightarrow{V_A = 38.66\text{ V}} 38.66\text{ V} - V_B = 13.4\text{ V} \rightarrow V_B = 25.26\text{ V}$$

The potential difference between "B" and "C" is:

$$V_B - V_C = I * R = 0.67\text{ A} * 28\ \Omega = 18.76\text{ V}$$

The potential (voltage) at "C" is:
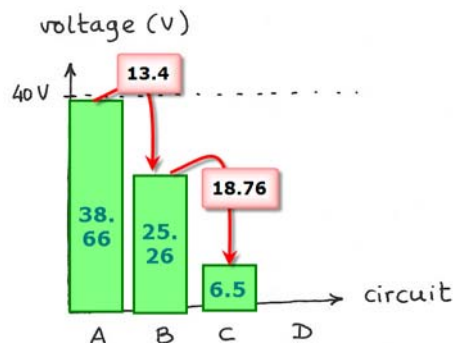
$$V_B - V_C = 18.76\text{ V} \xrightarrow{V_B = 25.26\text{ V}} 25.26\text{ V} - V_C = 18.76\text{ V} \rightarrow V_C = 6.5\text{ V}$$



### Determination of powers

The electric power (energy per second) supplied by the battery is:

$$P_{\text{supplied}} = \varepsilon * I = 40 \text{ V} * 0.67 \text{ A} = 26.8 \text{ W}$$


The power dissipated (as heat) by each resistor is:

$$P_r = I^2 * R = (0.67 \text{ A})^2 * 2 \Omega = 0.9 \text{ W}$$

$$P_{R1} = I^2 * R = (0.67 \text{ A})^2 * 20 \Omega = 9 \text{ W}$$

$$P_{R2} = I^2 * R = (0.67 \text{ A})^2 * 28 \Omega = 12.6 \text{ W}$$
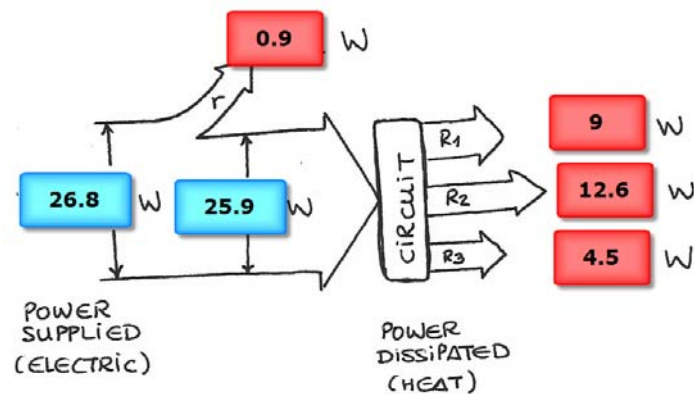
$$P_{R3} = I^2 * R = (0.67 \text{ A})^2 * 10 \Omega = 4.5 \text{ W}$$



### Determination of the readings

The reading of the ammeter gives the value of the current. The reading of the voltmeter gives the value of the potential difference between two points:

