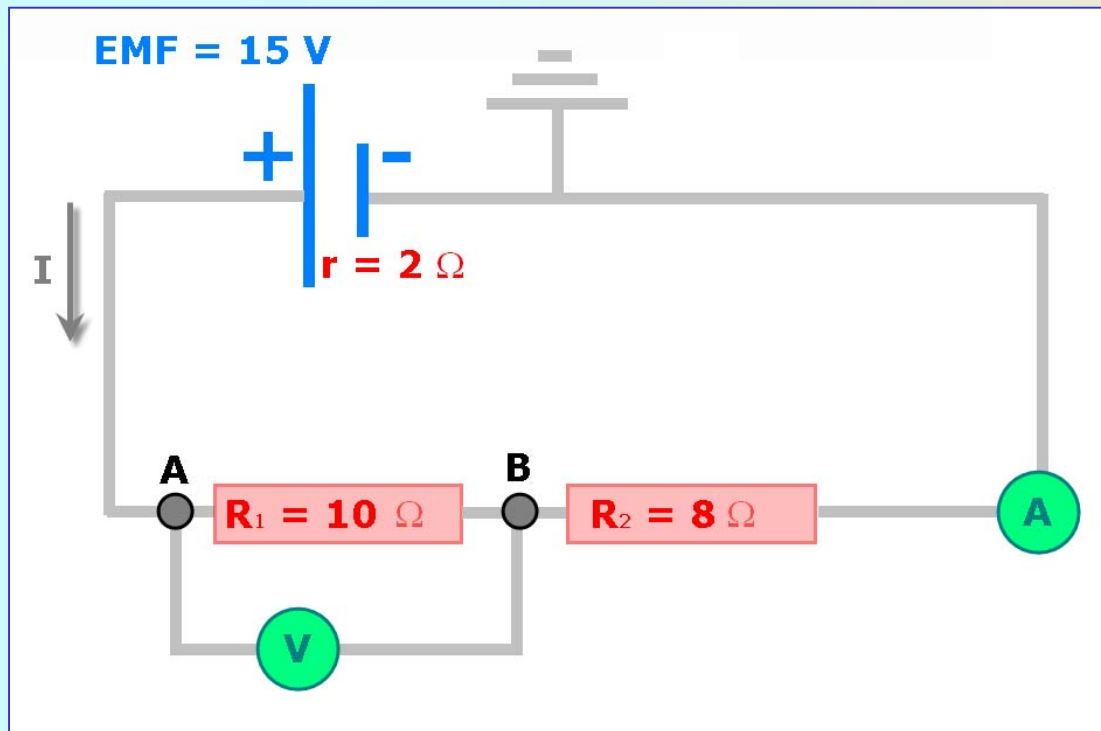


# Ohm's Law




## Exercise

In this electric circuit find:

- the equivalent resistance
- the current  $I$
- the voltage at point B
- the reading from the voltmeter ("V")
- the reading from the ammeter ("A")
- the power and heat dissipated by the resistor  $R_2$  in 10 hrs

# Ohm's Law

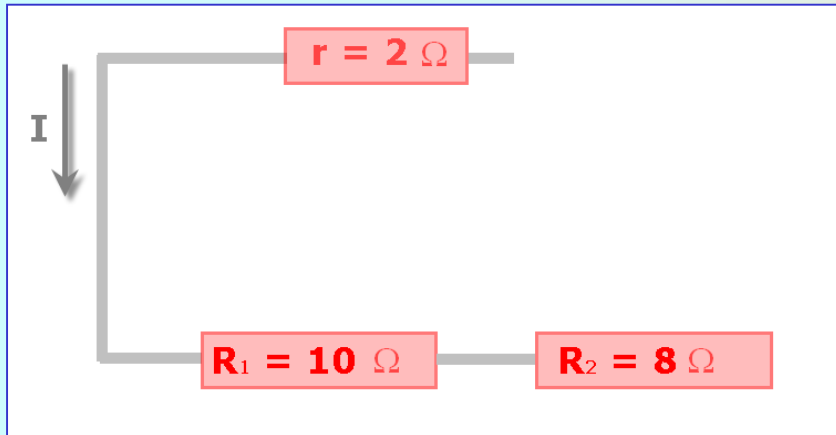

b) the current  $I$

According to Ohm's Law:

$$I = \frac{EMF}{R_{equiv}} = \frac{15 \text{ V}}{20 \Omega} = 0.75 \text{ A}$$

e) the reading from the ammeter ("A")

$$\text{reading of "A"} = 0.75 \text{ A}$$

## Solutions

a) the equivalent resistance

The three resistors (internal and the resistors in the circuit) are connected in series. When the resistors are connected in series, the equivalent resistance is:

$$R_{equiv} = r + R_1 + R_2 = 2 \Omega + 10 \Omega + 8 \Omega = 20 \Omega$$

c) the voltage at point B

In order to reach point "B" charges must overcome two resistances:  $r$  and  $R_1$ .

The change along a resistance can be calculated using this expression:


$$\Delta V = - I * R$$

In our case:

$$\Delta V = - 0.75 \text{ A} * (2 \Omega + 10 \Omega) = - 9 \text{ V}$$

$$V_B = V_{initial} + \Delta V = 15 \text{ V} - 9 \text{ V} = 6 \text{ V}$$

# Ohm's Law

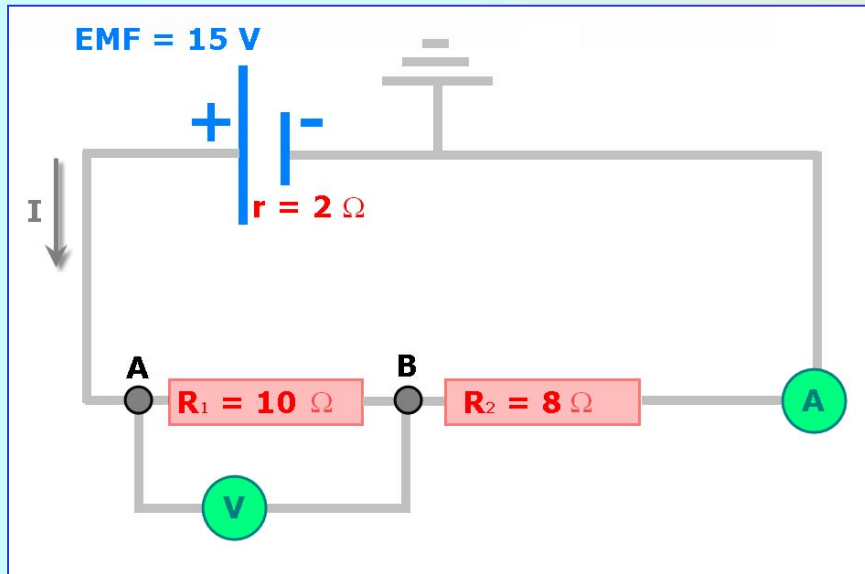

d) the reading from the voltmeter ("V")

The reading from the voltmeter corresponds to the change in voltage from point "A" to point "B":

$$V_A - V_B = -\Delta V = 0.75 \text{ A} * 10 \Omega = 7.5 \text{ V}$$

f) the power and heat dissipated by the resistor R2 in 10 hrs

$$\text{Power} = P = I^2 * R$$

$$P_{R2} = (0.75 \text{ A})^2 * 8 \Omega = 4.5 \text{ W}$$

Energy dissipated = Power \* time

$$E_{R2} = 4.5 \text{ W} * 36000 \text{ s} = 162000 \text{ J}$$

$$E_{R2} = 162000 \text{ J} \frac{1 \text{ kW-h}}{3600000 \text{ J}} = 0.045 \text{ kW-h}$$