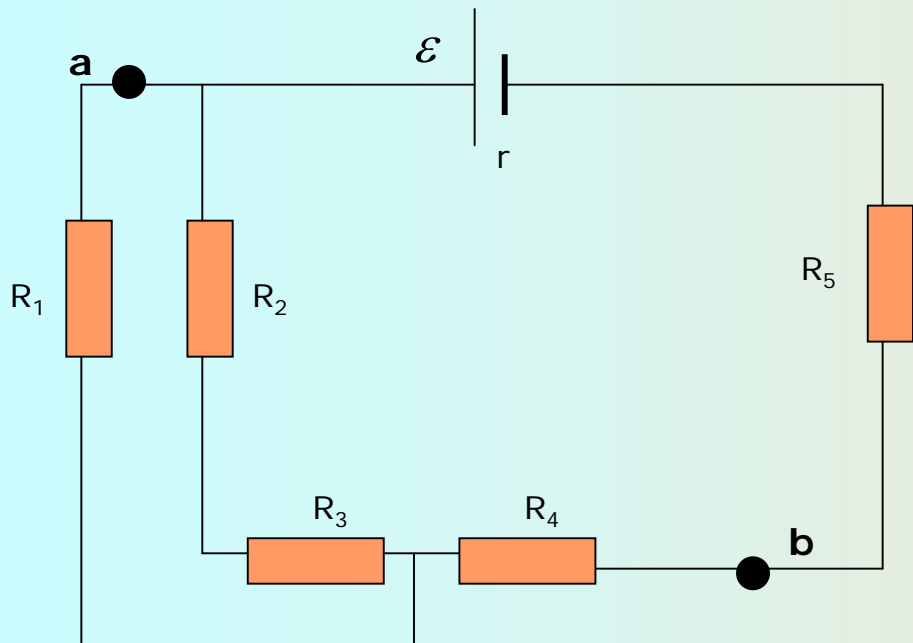


# Electric Circuit



In this electric circuit, find:

- a) the equivalent resistance
- b) the intensities of the current
- c) the potential difference  $V_a - V_b$

$$\mathcal{E} = 50 \text{ V}$$

$$r = 2 \Omega$$

$$R_1 = 10 \Omega$$


$$R_2 = 5 \Omega$$

$$R_3 = 8 \Omega$$

$$R_4 = 4 \Omega$$

$$R_5 = 6 \Omega$$

# Electric Circuit

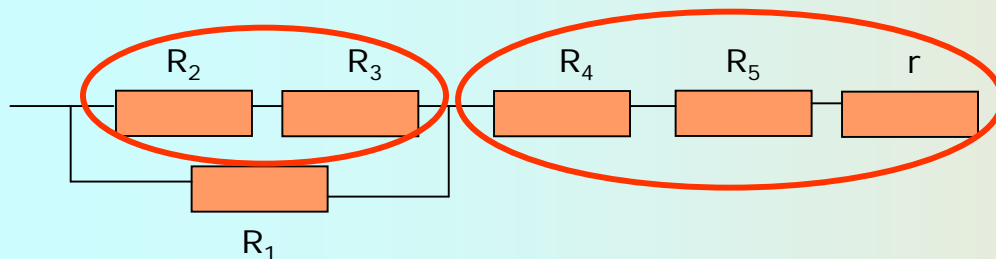

$$\varepsilon = 50 \text{ V}$$

$$r = 2 \text{ } \Omega$$

$$R_1 = 10 \text{ } \Omega$$

$$R_2 = 5 \text{ } \Omega$$

$$R_3 = 8 \text{ } \Omega$$

$$R_4 = 4 \text{ } \Omega$$

$$R_5 = 6 \text{ } \Omega$$

In this electric circuit, find:

a) the equivalent resistance


The resistors  $R_2$  and  $R_3$  are connected in series. Therefore, the resistance equivalent to both is:

$$R_{23} = R_2 + R_3 = 5 \text{ } \Omega + 8 \text{ } \Omega = 13 \text{ } \Omega$$

The resistors  $R_4$  and  $R_5$  are also connected in series. Therefore, the resistance equivalent to both is:

$$\begin{aligned} R_{45r} &= R_4 + R_5 + r = 4 \text{ } \Omega + 6 \text{ } \Omega + 2 \text{ } \Omega = \\ &= 12 \text{ } \Omega \end{aligned}$$

# Electric Circuit

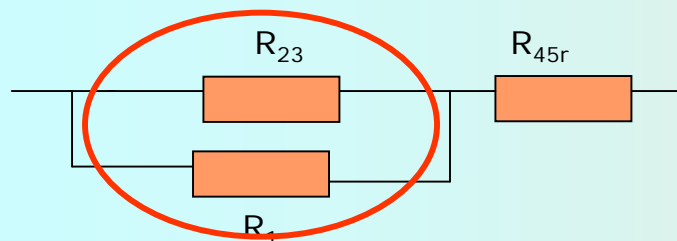

$$\mathcal{E} = 50 \text{ V}$$

$$R_{23} = 13 \text{ } \Omega$$

$$R_1 = 10 \text{ } \Omega$$

$$R_{45r} = 12 \text{ } \Omega$$

In this electric circuit, find:


a) the equivalent resistance

The resistors  $R_{23}$  and  $R_1$  are connected in parallel. The expression to determine the equivalent resistance is:

$$\frac{1}{R_{123}} = \frac{1}{R_1} + \frac{1}{R_{23}}$$

$$\frac{1}{R_{123}} = \frac{1}{10 \text{ } \Omega} + \frac{1}{13 \text{ } \Omega} = \frac{13 + 10}{130 \text{ } \Omega} = \frac{23}{130 \text{ } \Omega}$$

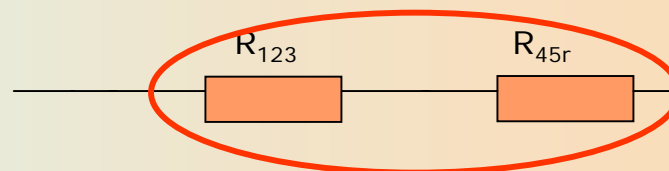
$$R_{123} = \frac{130 \text{ } \Omega}{23} = 5.65 \text{ } \Omega$$



The resistors  $R_{123}$  and  $R_{45r}$  are connected in series. Therefore, the resistance equivalent to both is:

$$\begin{aligned} R_{\text{equiv}} &= R_{123} + R_{45r} = \\ &= 5.65 \text{ } \Omega + 12 \text{ } \Omega = \\ &= 17.65 \text{ } \Omega \end{aligned}$$

# Electric Circuit

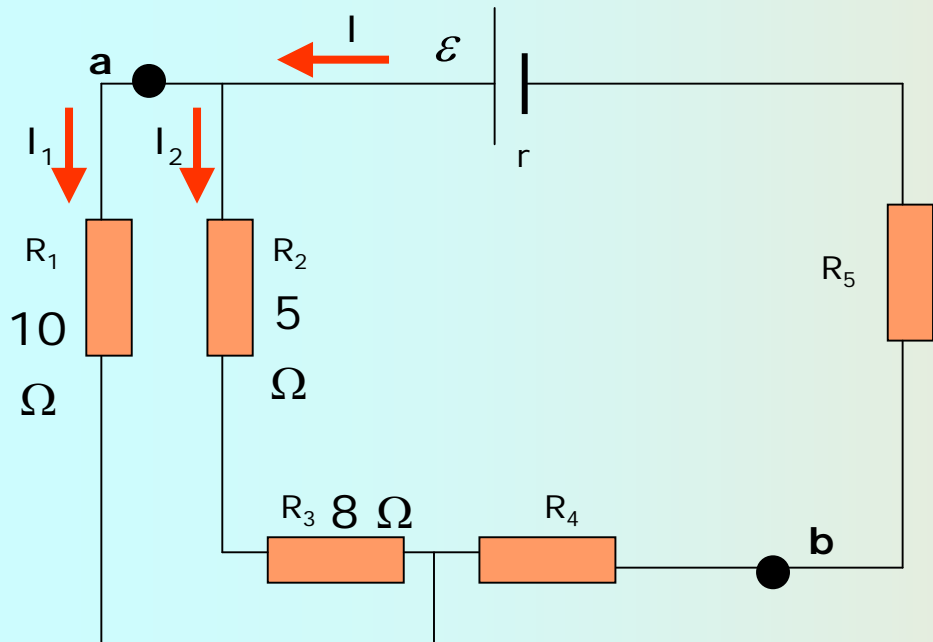

In this electric circuit, find:

b) the intensities of the current

The total current can be calculated applying Ohm's Law:

$$I = \frac{\varepsilon}{R_{\text{equiv}}} = \frac{50 \text{ V}}{17.65 \Omega} = 2.83 \text{ A}$$


The current in each branch can be calculated by solving this system:

$$\varepsilon = 50 \text{ V}$$

$$R_{\text{equiv}} = 17.65 \Omega$$

$$\begin{cases} i_{1\text{st branch}} + i_{2\text{nd branch}} = I \\ i_{1\text{st branch}} * R_{1\text{st branch}} = i_{2\text{nd branch}} * R_{2\text{nd branch}} \end{cases}$$

# Electric Circuit

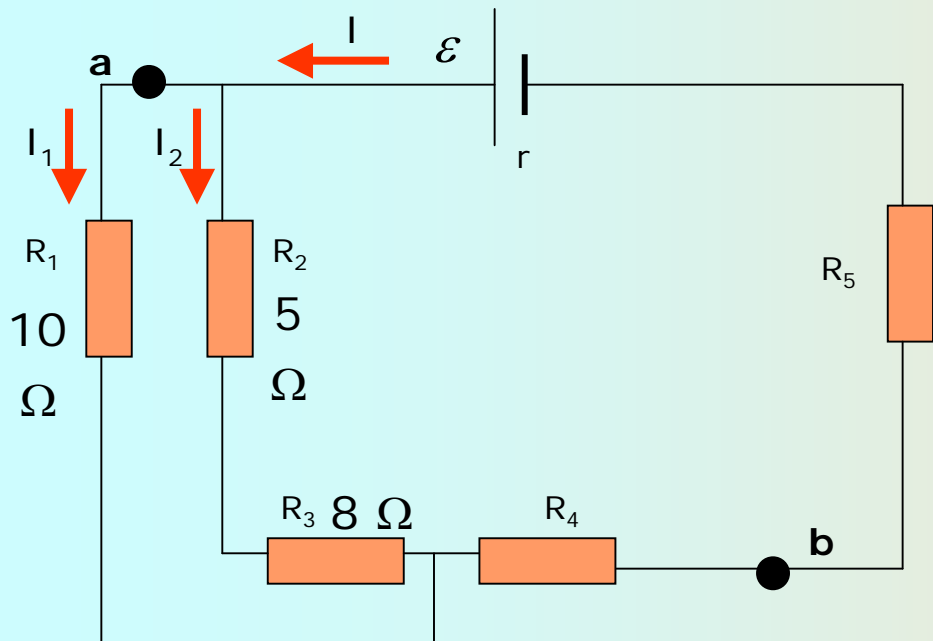

$$\varepsilon = 50 \text{ V}$$

$$R_{\text{equiv}} = 17.65 \Omega$$

In this electric circuit, find:

b) the intensities of the current

In our case:

$$\begin{cases} i_1 + i_2 = 2.83 \text{ A} \\ i_1 * 10 \Omega = i_2 * 13 \Omega \end{cases}$$


By substitution:

$$i_2 = 2.83 - i_1 \rightarrow i_1 * 10 = (2.83 - i_1) * 13$$

$$\rightarrow 10 i_1 = 36.8 - 13 i_1 \rightarrow 23 i_1 = 36.8$$

$$\rightarrow i_1 = \frac{36.8}{23} = 1.6 \text{ A} \rightarrow i_2 = 2.83 \text{ A} - 1.6 \text{ A} = 1.23 \text{ A}$$

# Electric Circuit

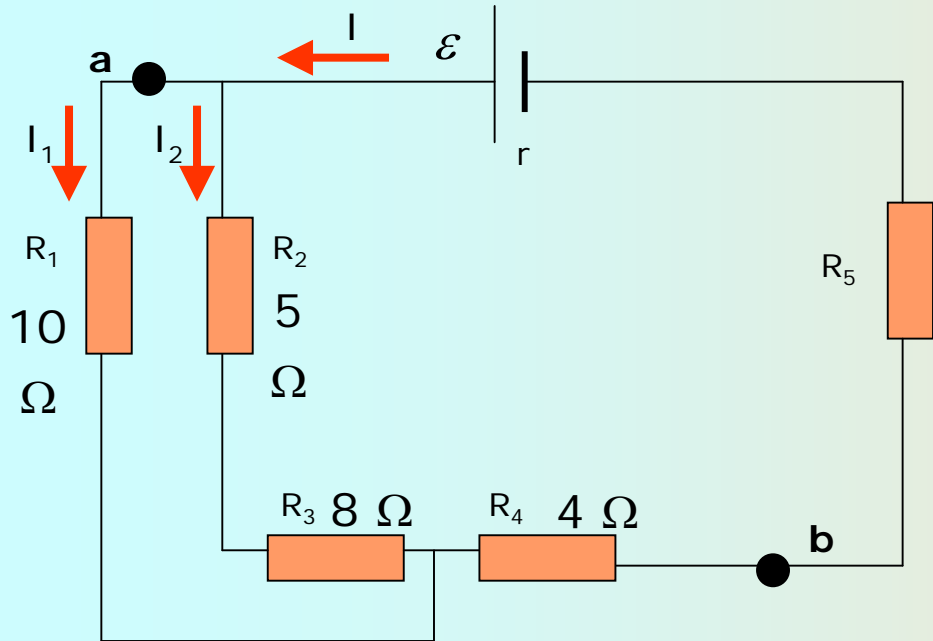

$$\varepsilon = 50 \text{ V}$$

$$R_{\text{equiv}} = 17.65 \Omega$$

In this electric circuit, find:

c) the potential difference  $V_a - V_b$

$$\begin{aligned}
 V_a - V_b &= 1.6 \text{ A} * 10 \Omega + 2.83 \text{ A} * 4 \Omega \\
 &= 1.23 \text{ A} * 13 \Omega + 2.83 \text{ A} * 4 \Omega \\
 &= 2.83 \text{ A} * 5.65 \Omega + 2.83 \text{ A} * 4 \Omega \\
 &= 27.3 \text{ V}
 \end{aligned}$$